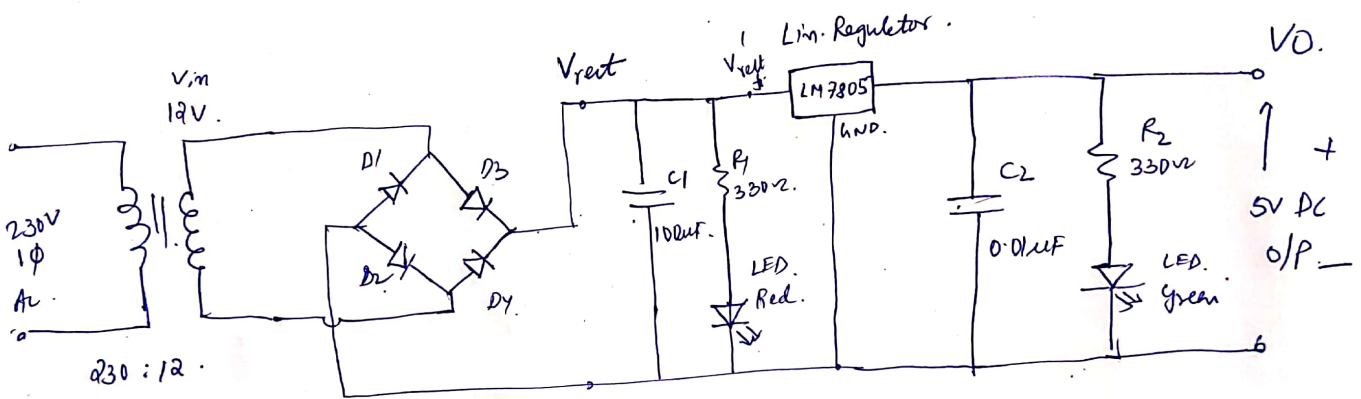


5V DC power Supply Chk



Diodes \rightarrow 1N4007

Linear Regulator \rightarrow LM 7805.

T/F turns ratio \rightarrow 230:12

Waveforms

