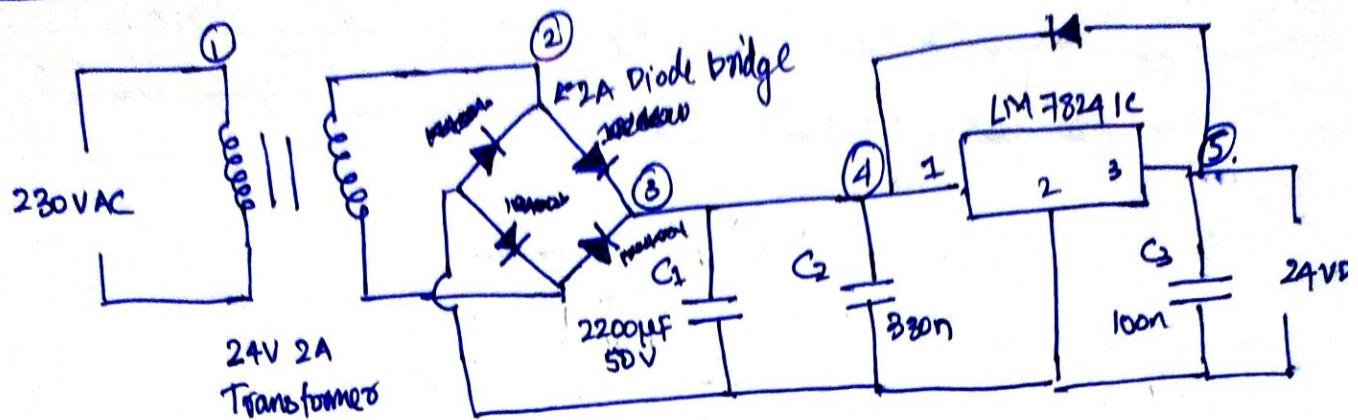







Power Supply Summary

230V AC to 24V DC power supply

IN4001



Voltage Waveforms

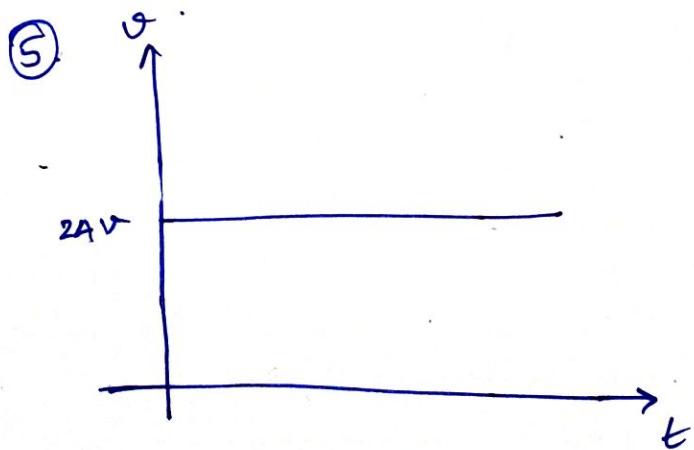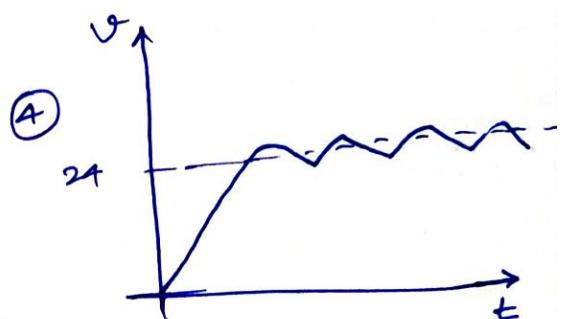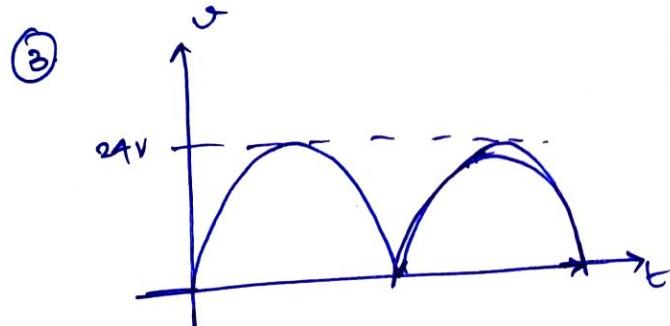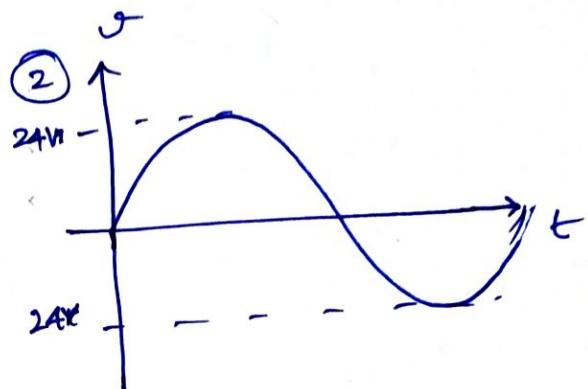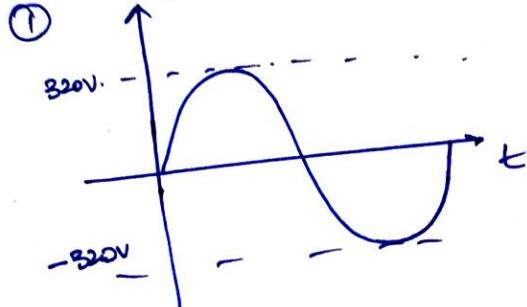

For 230V AC to 05V DC conversion we can use same circuit with 230V AC to 5V transformer and LM7805 IC.

⇒ On board

- On board AC to DC regulated power supply modules are available in market.
- For 230V AC to 0.5 V DC power to MCUs, we can use Hi-Link 5V/5W power converter module.