

[Prasad Reddy]

[190020018]

## System Design of Electronic Product (Endsem)

Summary of how I approach the given  
Design problem:

Given a gas detection sensor (Honeywell EC-FX Ammonia gas sensor), I need to detect and alert when ammonia concentration exceeds 100 PPM in atmosphere.

→ Since as per datasheet, its a current output sensor, with the output current proportional to the ammonia gas concentration in PPM, and given that there are 3 variants of sensors, 0-100, 0-200, 0-250 PPM  $\text{NH}_3$ . My design choice would be to go with 0-200 PPM  $\text{NH}_3$  sensor since the threshold we want to detect (100 PPM) lies in the midway of range 0-200 PPM.

→ And then, ~~the~~ I'll be converting this output current into voltage by ~~the~~ connecting appropriate valued resistor in series with sensor output terminal and measure the output voltage across it.

→ As per the given datasheet, it says Baseline offset (for clean air) is  $0.2 \text{ mA}$ , and sensitivity is  $100 \pm 40 \text{ nA/ppm}$ .

→ As I'll be using  $0-200 \text{ PPM NH}_3$  range gas sensor, assuming output current is  $0.2 \text{ mA}$  at  $0 \text{ PPM}$  (clean air), considering the average sensitivity of  $100 \text{ nA/ppm}$  the output current at our required threshold of  $100 \text{ ppm}$  is

$$(0.2 \text{ mA}) + (100 \times 100) \text{ nA} = 0.21 \text{ mA}$$

→ Considering the worst case sensitivities  $(100+40) \text{ nA/ppm}$  and  $(100-40) \text{ nA/ppm}$  we have sensitivities as  $140 \text{ nA/ppm}$  and  $60 \text{ nA/ppm}$ .


→ For  $140 \text{ nA/ppm}$ , output current at  $100 \text{ ppm}$  is  $[(0.2 \text{ mA}) + (100 \times 140) \text{ nA}]$   
 $= (0.2 \text{ mA} + 0.014 \text{ mA}) = 0.214 \text{ mA}$

→ For  $60 \text{ nA/ppm}$ , output current at  $100 \text{ ppm NH}_3$  is  $[(0.2 \text{ mA}) + (100 \times 60) \text{ nA}]$   
 $= (0.2 \text{ mA} + 0.006 \text{ mA})$   
 $= 0.206 \text{ mA}$

→ So, basically <sup>for</sup> our threshold at  $100 \text{ ppm NH}_3$ , output current is somewhere between  $(0.206 \text{ mA} - 0.214 \text{ mA})$  depending on sensitivity. And since these are too small values, I'm choosing the resistance value as  $10 \text{ k}\Omega$  so that the voltage across the resistance ranges in  $(0.206 \text{ mA}) \times (10 \text{ k}\Omega) - (0.214 \text{ mA}) \times (10 \text{ k}\Omega)$   
 $= 2.06 \text{ V} - 2.14 \text{ V}$  for  $100 \text{ ppm NH}_3 \text{ conc.}$

→ But since safety is the first priority here, I'll be going with lowest value of 2.06 V for the ~~threshold~~ threshold 100 ppm  $\text{NH}_3$  conc.

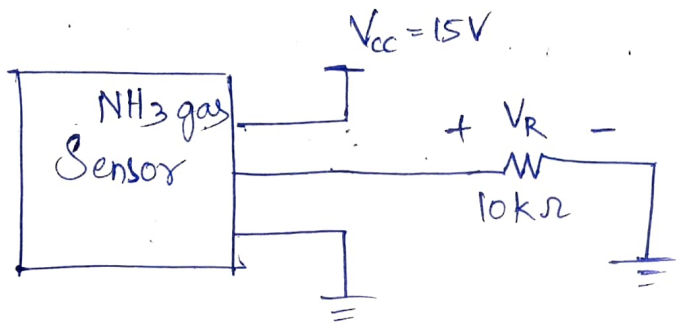
→ It implies that if the ~~output~~ voltage across that series resistor with sensor exceeds 2.06 V, it raises buzzer/ alarm.



if  $V_R > 2.06V \Rightarrow$  raise alarm / buzzer  
else  $\Rightarrow$  do nothing and relax :)

→ For achieving this, I'll be using <sup>LM741</sup> opamp as comparator ( $V_{cc} = 15V$ ) with reference voltage given as 2.06V.

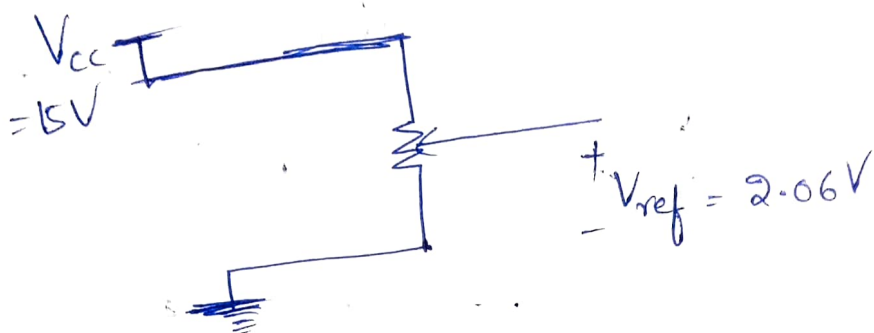→ For achieving the reference voltage  $2.06\text{V}$ , I'll be using a simple voltage divider circuit ~~as below~~ and a potentiometer)



→ And importantly, all the resistors I'll be choosing will be the ones with least tolerance values ( $\pm 5\%$ ) so that our calculations won't go too wrong/bad in the worst case scenarios.

→ And finally, the output of this comparator is connected to a red LED as well as a piezoelectric buzzer (which is a DC buzzer, works with DC voltage) for visual and audio alarms respectively to alert if  $\text{NH}_3$  conc. is higher than  $100\text{ ppm}$  in atmosphere.