

2. Ammonia sensor: EC-HX-NH₃ sensor


Given specifications in question: Alert when concentration > 100 ppm

For a range of 0-100 ppm, 25 ppm is the default alarm level

Here we want alarm at 100 ppm, we'll need 0-400 ppm range

EC-HX-NH₃ sensor specifications

Range - 0-500 ppm

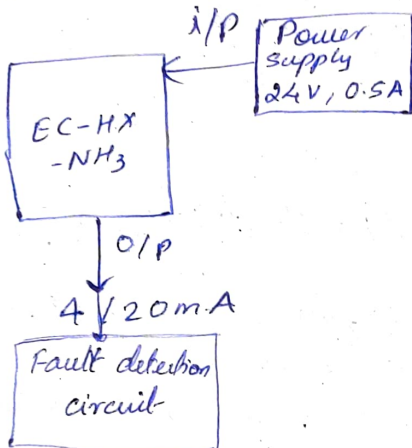

Fault level < 10 ppm
↓
0.5 mA


Maximum input impedance of monitoring equipment = 700 Ω

$$\Rightarrow \begin{array}{ccc} I & R & V \\ 4 \text{ mA} & 700 \Omega & 2.8 \text{ (V}_{\text{min}}) \\ 20 \text{ mA} & 700 \Omega & 14 \text{ (V}_{\text{max}}) \end{array}$$

Requirements:

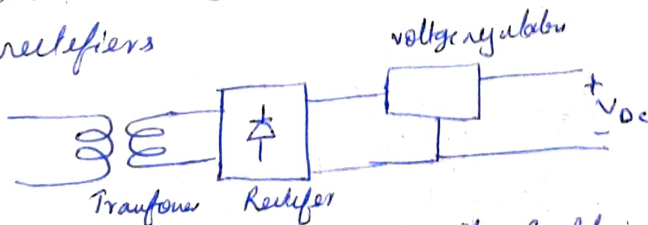i) **Power supply**: An isolated DC power supply of rating 24V, 0.5A $\Rightarrow P = 12 \text{ W}$ supply

- Implement using DC-DC converter: For DC-DC converters, we have certain disadvantages like they are prone to noise, duty cycle control, switching frequency
- Implement using transformers, voltage regulators and rectifiers



Use of transformers makes it bulkier and can lead to electromagnetic interference issues, makes it costly.

Keeping a transformer inside the product will increase the weight and size of the product

Solution:

Use an isolated AC-DC power supply module which converts 230V (AC) to 24V (DC). It is already available in market

HLK-20M24 \Rightarrow Isolated AC-DC power supply

Advantages: \rightarrow Compact
 \rightarrow Easier use
 \rightarrow No external control
 \rightarrow Less costly


2) Monitoring equipment / Fault detection circuit

Requirement \rightarrow When atmospheric concentration of ~~equal~~ ammonia is equal to or greater than 100ppm, then an alert should be sent

The ~~an~~ available sensor is a current sensor, therefore we need to either convert to voltage or current. Current sensors are prone to offsets, negative & positive gains, defects in case of sensors etc. And so, it is easier to convert to voltage and then detect if the obtained voltage is corresponding to a fault concentration above 100ppm

Current to voltage converter

1) Transimpedance amplifier

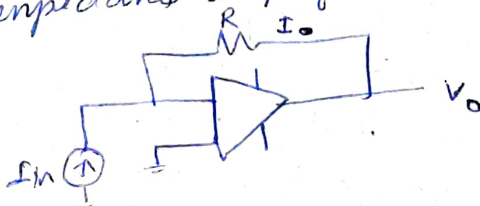

In the figure shown above, the current I_{in} is the one from sensor which is given as input to an Op-amp. The feedback resistor ~~which~~ will have a drop of $I_{out} \times R$ which will be same as V_o ($V_o = -I_{out} R$) (Due to virtual ground concept, $I_{in} = I_{out}$) So now voltage is obtained but the next stage will also be a voltage det detection of fault voltage using Op-amp.

Problem: If we use Op-amps we will need different biasing which will complicate the circuit and making it bulkier.

ii) Current to voltage converter can be simply done using a resistor, but we have to ensure that power loss is minimum.

As per sensor specifications, minimum input impedance is 700Ω . But we want to design this resistor as per the voltage required.

3) Matching the sensor specification to monitoring equipment

Sensor characteristics:

⇒ When concentration is less than 10ppm, it is faulty region. which means 10ppm is minimum value

Also it is given that 0.5mA is faulty current

∴ $10ppm \Rightarrow 0.5mA$

Range of operation: 0 - 500ppm


current output: 4 - 20mA

Description: Sensor behaves in a linear fashion

∴ For 10ppm $\Rightarrow 0.5mA$

500ppm $\Rightarrow 20mA$

Then for 100ppm \Rightarrow it is 4mA

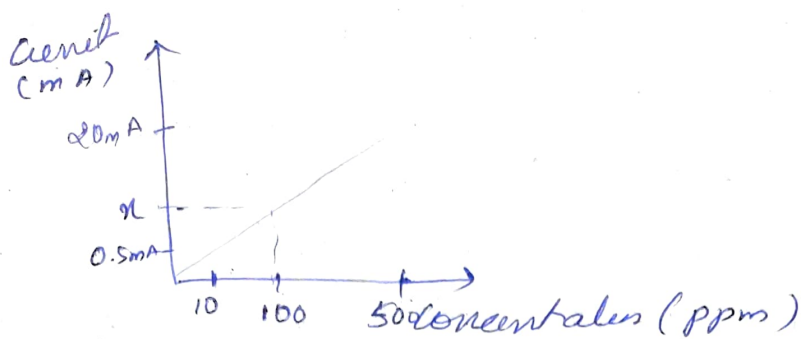

∴ For a concentration of 100 ppm \Rightarrow Current is 4 mA

Resistor selection

Voltage drop across the resistor across the sensor is given as the input to Op-amp Differential amplifier. If 'R' is too low, that means the reference voltage for differential amplifier should also be same.

In hand: The biasing for the differential amplifier is given through the DC supply used for sensor (24V). Using this same 24V, we can generate the reference (-ve terminal of Op-amp) as well as biasing for the Op-amp.

∴ We have to choose an 'R' such that voltage drop across 'R' can be generated from the 24V supply



$$\text{At } 100 \text{ ppm of } R = 700 \Omega \left. \begin{array}{l} I = 4 \text{ mA} \\ V = 2.8 \text{ V} \end{array} \right\} P_{\text{loss}} = 11.2 \text{ mW}$$

$$\text{of } R = 500 \Omega \left. \begin{array}{l} I = 4 \text{ mA} \\ V = 2 \text{ V} \end{array} \right\} P_{\text{loss}} = 8 \text{ mW}$$

This 2V will be the reference for differential amplifier which is generated from 24V

If 2.8V is to be the reference:

If 2V is the reference

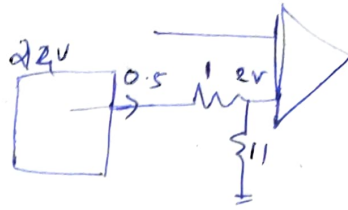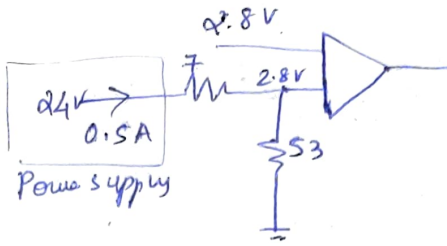

$$P_{(7\Omega)} = 1.75W$$

$$P_{(53\Omega)} = 13.25W$$

$$P_{(0.5\Omega)} = 0.5W$$

$$P_{(11\Omega)} = 2.75W$$



Power loss is more when we choose 2.8V as the reference

∴ 2V will be the reference

⇒ 2V should come out of sensor which is indicating the 100ppm concentration


$$R = 500\Omega$$

4) Final circuit

- Sensor will detect the concentration, if the concentration is equal to or greater than 100ppm it sends a current of 4mA and above
- This current will flow through the input resistance of monitoring equipment and the voltage across this resistance will be given to differential amplifier.
- The Op-amp input will be a reference voltage at -ve terminal & the output of 'R' will be given at +ve terminal of Op-amp, whenever $V_+ > V_-$

$$V_o = A_{OL}(V_{bias})$$

A_{OL} - gain of Op-amp

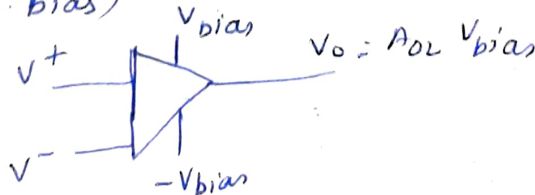

The Op-amp chosen is LM6211 whose specs are

Input bias voltage: 24V

Maximum differential voltage: ~~0.1V~~ $\pm 0.3V$

Circuit diagram:

The output of Op-amp will be connected to a sensor and LED, depending on current of Op-amp (typically max. current) $-0.25mA$

$$V_{out} = 24V$$

$$\Rightarrow R = \frac{24}{0.25m} = 96k \approx 100k$$

Circuit diagram:

