
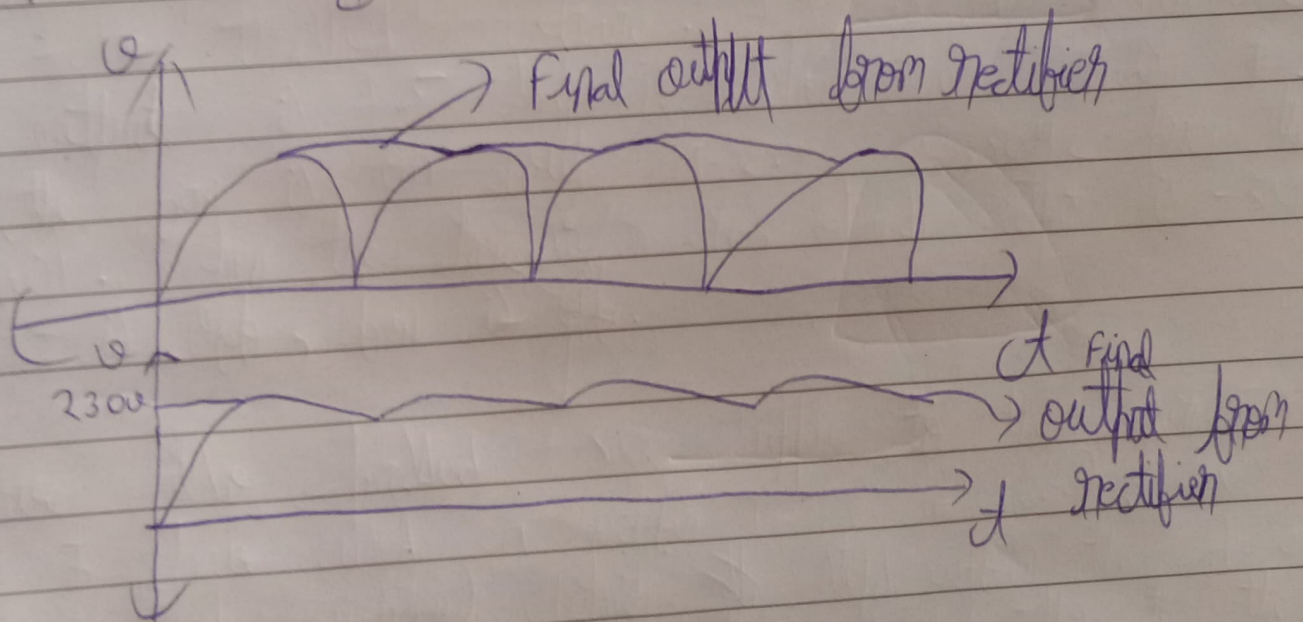


Date : _____

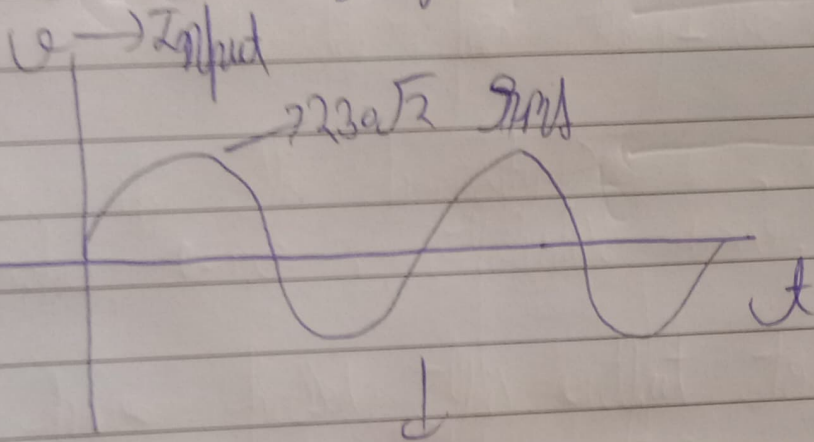Q. 4) To get the 230V 50Hz for the fan voltage from the main had to be used. I have also used it for the rest. I have used a battery to get 1860 mV at the op-amp-10e terminal. I have then used the same main voltage and converted it to D.C. using a rectifier.



Date : _____

↳ works with feedback

↳ The above down to source and back
concepts finally to SW. This is passed to the server
and the app device must be connected to main at all times to
work.

↳ It is passed directly
into the tree SW
side and through
an interface in
the -ve side.

↳ Final output (print or log)