

System Design of Electronic Products

End sem


: Shivam Kumar

180020034

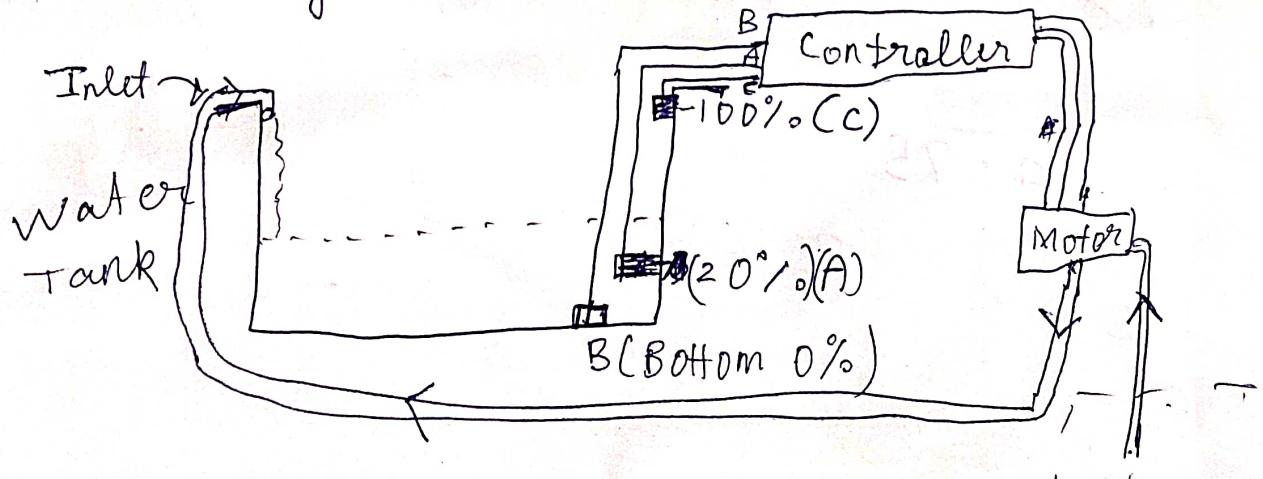1) So basically when the water in tank is above 20% the circuit is completed between A & B and as soon as water falls below 20%, the circuit A & B is disconnected and then pump shall start. When circuit B & C is completed that means tank is full and pump shall stop.

To make this sensor fail safe we shall ensure ~~not~~ to use long lasting components and ~~fising~~ sensors

B (at bottom of tank), A (at 20% mark) C (at 100% mark of tank) such that they dont fall off due to water or other factors ~~like~~ like corrosion which may break the clamps and sensors.



System Constraints:

Input voltage = 230 V AC.

Motor Power = ~~80W~~ 1 KW

Max motor current ~~2.12A~~ 2.51A

so our relay shall be capable of handling ~~3A~~ A under normal cases.

We use Platinum Electrodes for that

We have to turn on when Port(A) is high and turn off when A and C are both high.

Port B is at Vcc (12V)

(In case the tank size is big then very small check voltage may cause errors.)